

# POWER FACTOR TESTING OF POWER TRANSFORMERS

By O. W. Iwanusiw  
AVO MULTI-AMP CANADA LIMITED

## GENERAL

Power factor testing of electrical insulation is one of the recognized and highly-regarded procedures in the preventive maintenance process of electrical power apparatus. The power factor of electrical insulation, the ratio of the power loss to the volt-amperes, is a measure of the quality of the insulation. The lower the power factor, the better the condition of the insulation. With this in mind, the electrical power industry is monitoring the power factor of their major system components to avert unwanted failures and outages.

This paper will consider the requirements for equipment to be used for power factor testing, comment on available equipment, discuss problems of interference and outlines procedure and readings to be taken on two-and-three winding transformers.

## TEST EQUIPMENT REQUIREMENTS

To say that the test equipment has to measure the power factor of electrical insulation would be greatly oversimplifying the problem. To put the problem in a better prospective one should list and discuss the requirements of the test equipment for this application.

- The test equipment must measure capacitance and power factor of electrical insulation. A measurement of the dissipation factor or power loss is also acceptable, as the power factor can be readily calculated from these values.
- The test equipment must measure insulation that is grounded (GST test) or ungrounded (UST test). This is a real necessity, as practical applications demand such measurements.
- The test equipment must be equipped with an effective guard circuit. As most practical applications involve several interconnected capacitors, it is necessary to separate these into individual sections for analysis. The only practical method of doing this is to be able to eliminate them from the measurement by suitable guarding.

It should be pointed out that there are two types of guard circuits possible. In the HOT GUARD configuration the guard is at the test potential of the test set. In the COLD GUARD configuration the guard is at, or near, ground potential. As the HOT GUARD configuration requires more diligence on the part of the operator, with respect to safety, the COLD GUARD circuit is usually preferred.

- The test equipment must reject or cancel interference. Most practical situations involve measurements near live lines or other power equipment. Such live apparatus invariably interfere with measurements by injecting power frequency interference into the measuring circuit. To allow measurements in the presence of interference, the equipment must have provisions for rejecting or cancelling interference.
- The test equipment must be capable of conducting measurements at the traditional stress levels. As most people in the industry have been making measurements typically at 10 or 2.5 kV, the test equipment must be capable of duplicating these measurements so as not to disturb trend analysis.

## AVAILABLE TEST EQUIPMENT

The equipment available for conducting power factor testing is varied. Most of the traditional test equipment were bridges such as the Shering Bridge and the Transformer Ratio Arm Bridge. These are shown in Figure 1 and 2, respectively. Both of these measure the dissipation factor of the insulation being measured,

rather than the power factor. The difference between the power factor and the dissipation factor, however, is very small, especially for insulation of good quality, that is for power factors less than 5%. The Transformer Ratio Arm Bridge circuit is more suitable for this application as it offers guard connection that is inherent to the circuit and passive in nature.

To use the above bridge circuits for the measurement of grounded specimen (GST test) such measuring equipment must use double shielded power sources, as well as double shielded high-voltage cables. Only in this way can power line interference and internal residuals be reduced to a value that permits a meaningful measurement.

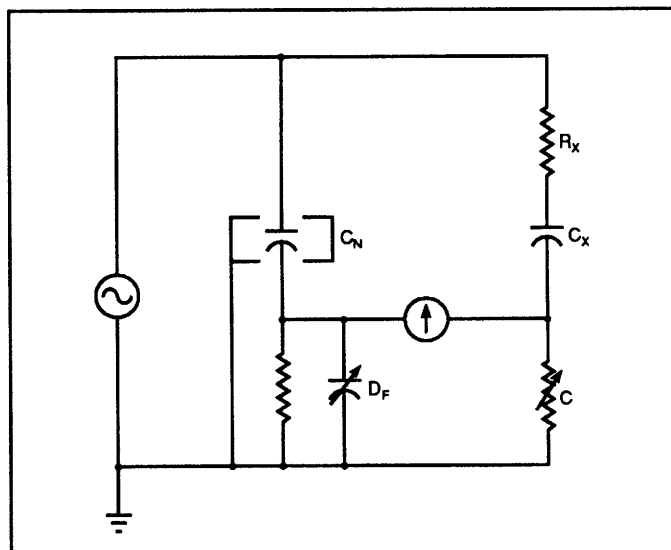


Figure 1. Schematic of a Shering Bridge

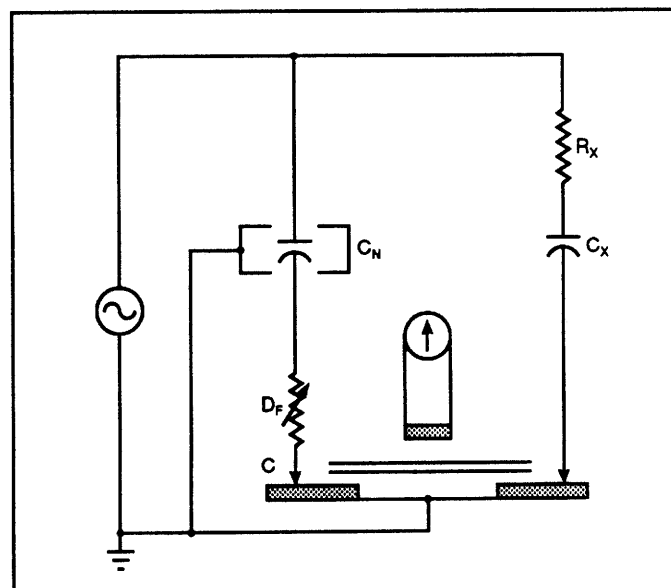


Figure 2. Schematic of a Transformer Ratio Arm Bridge

Over the years many pieces of test equipment were developed and used for this application. Perhaps the most famous of these is the Doble Power Factor Test Set. A simplified diagram of this test set is shown in Figure 3. In reality, this piece of test equipment does not measure power factor, but it does allow the user to calculate the power factor from two measurements. The first measurement is the total current in the measuring circuit. The second measurement is the residual current, after all the quadrature current is subtracted, or cancelled, from the measuring circuit.

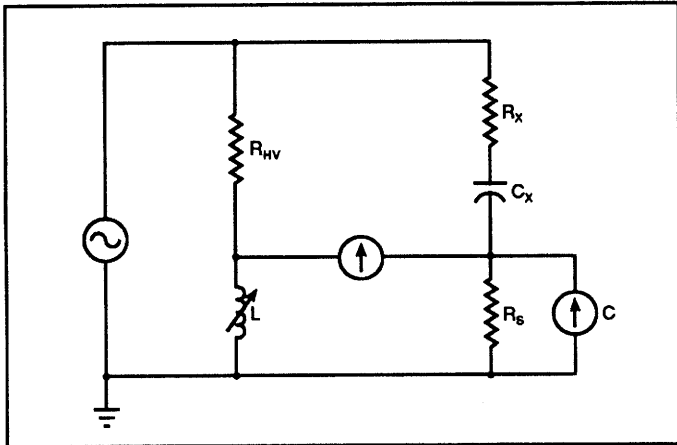


Figure 3. Schematic of a Doble Power Factor Test Set

It is noteworthy to point out that if such a test set is operated at a reference voltage, say 10,000 volts, then the total current in the measuring circuit is proportional to the capacitance of the insulation and the residual current in the measuring circuit is proportional to the power loss. The ratio of the residual to the total current is the power factor of the insulation being measured. Being a readout type instrument, this test set has few controls and is simple to operate.

The Doble set is not without its shortcomings. Consisting of resistances, inductance and capacitance, the test set is sensitive to frequency and accentuates harmonics in the measuring circuit. It must rely on filtering to provide the desired reading.

There are a variety of other developments, each with its advantages and disadvantages. There is the "Cameron Hot Box" shown in Figure 4. This is an Inverted Shering Bridge, where parts of the instrument are at high voltage and the controls are operated with the aid of insulating shafts. Its uniqueness is the use of the internal capacitance between the internal bridge components and the outside case for the reference capacitor. Its shortcomings are its inability to measure ungrounded specimen and the absence of a guard connection.

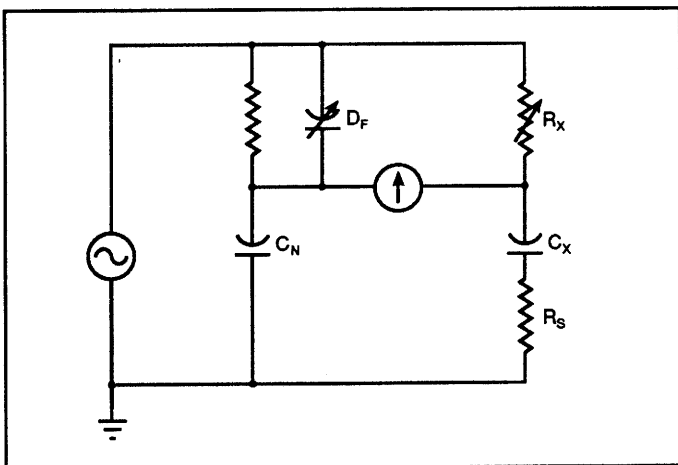


Figure 4. The Inverted Shering Bridge - The Cameron Hot Box

There is the Olman Instruments CB60. This is a transformer ratio arm bridge circuit, of the HOT guard configuration, which could be operated in UST and the GST connections. To operate in the GST connection, the instrument is insulated from ground and the controls are operated by means of insulated shafts, similar to the inverted Shering bridge. This instrument has impressive features such as an effective guard for both UST and GST connections and interference suppression circuitry. Its downfall was the HOT GUARD circuit whose voltage was 10,000 volts when the instrument was operated at 10,000 volts in the GST connection. Figure 5 shows the CB60 in the GST connection. This characteristic made the instrument rather unsafe.

There are other transformer ratio arm bridge circuits introduced by Olman Instruments and Tettex Instruments. All of these feature the COLD GUARD circuit, where the potential of the guard is at or very near ground potential. These instruments are considered to be safer than the HOT GUARD, and therefore readily accepted by the industry. The problem with most of these test sets is that they are full ac bridges, and as such require balancing of the in phase and quadrature components. Under usual field conditions, which may require an adjustment to suppress power frequency interference, the balancing procedure gets to be rather involved. These operating complications are responsible for these instruments not being widely accepted by the industry.

One very desirable characteristic of the transformer ratio arm bridge is that it can be easily configured to cancel or suppress interference. The interference could be reduced, or even eliminated, by injecting current from an internal or external source to one of the windings on the transformer.

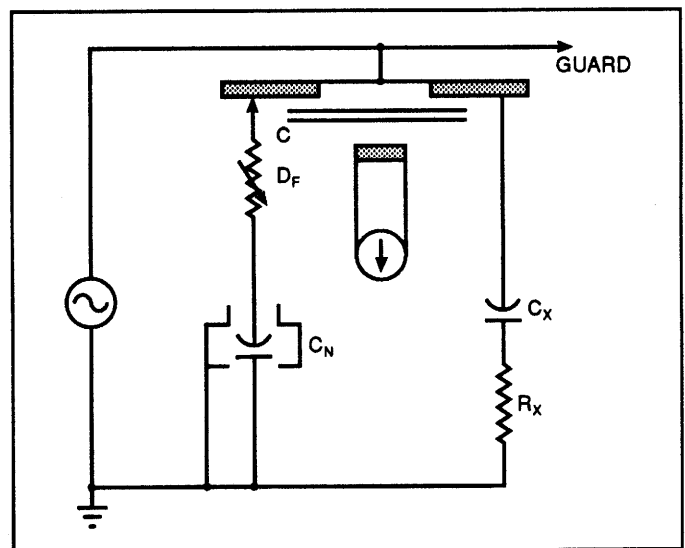


Figure 5. A HOT GUARD Transformer Ratio Arm Bridge

A general characteristic of all bridges is that they are designed to test insulation of relatively low power factors, say below 10%. They are not designed for the measurement of equipment exhibiting high power factors. Lightning arresters, for example, are typically very difficult if not impossible to measure on some bridges, as they may fall outside of the dissipation factor range. This is a definite drawback not only for the transformer ratio arm bridge, but for all capacitance bridge circuit in general.



The suppression technique is typically limited to a signal to interference ratio of 1 in the measuring set up. Above this level precise correlation techniques and circuits with extreme linearity must be employed. The ratio of signal to interference ratio that can be tolerated will depend on the linearity of the measuring circuitry.

### Interference Cancellation.

There are at least two ways of applying cancellation techniques to reduce the effect of interference on the measurement. One of these is to make two measurements, one with forward and one with reverse polarity of the test voltage, and then to average the results to obtain the final reading. As a result of this simple procedure the effect of the interference signal will be greatly reduced or even completely eliminated. This arrangement is simple, convenient, and is applicable to situations where the interference is small, say less than 10% of the total current. Good readings can be obtained even at higher interference levels, provided that the interference is very steady and that the measuring circuit is very linear.

For situations where the interference is higher, say more than 10%, other techniques must be used. One of these is interference reduction by cancellation. As was mentioned earlier, the transformer ratio arm bridge circuit is very convenient for this as it allows the application of a current to any of the windings on the bridge transformer.

In practice, the interference current is measured and a current of the same magnitude but of opposite polarity is injected into the bridge transformer. If accurately done, the interference will be substantially reduced. Some complications with this principle arise due to the stability of the interference and the stability of the cancelling current.

It is not the intention of typical cancellation circuits to eliminate the interference completely. A measurement with forward and reverse test voltage polarity still must be done to obtain a good reading. Interference cancellation principles, together with reading averaging, make it possible to make measurements in situations where the interference is thousands of percent higher than the signal to be measured.

## SPECIMEN TO BE MEASURED

As this presentation is focused mainly on the maintenance of transformers, we will consider the measurement of a two winding transformer, the measurement of a three winding transformer and the measurement of bushings.

To facilitate the measurement of insulation power factor, most transformers have all of their windings terminated on bushings even if one of them may be directly grounded. To measure the bushings, these are typically equipped with "Test Taps" that allow the bushings to be measured without disconnecting them from the transformer.

### Two Winding Transformers.

The simplified schematic diagram of a two winding transformer is shown in Figure 7. It consist of three components, namely:

- the high-voltage winding to ground capacitance ( $C_{H-g}$ ),
- the high-to-low voltage winding capacitance ( $C_{H-l}$ ),
- the low-voltage winding to ground capacitance ( $C_{L-g}$ ).

The capacitances listed above include the capacitance of the bushings. As the bushings are connected to ground, the high-voltage winding to ground measurement will include the capacitance of the high-voltage bushings. Similarly, the low voltage to ground measurement will include the capacitance of the low-voltage bushings.

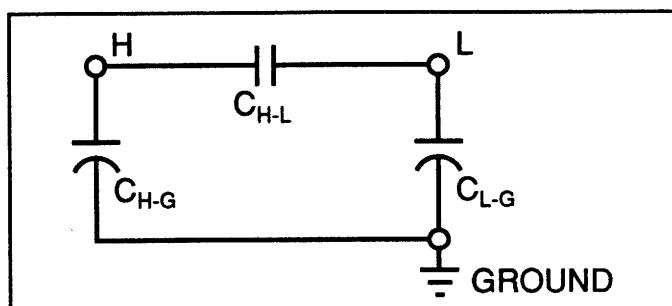


Figure 7. Schematic of a Two Winding Transformer

### Three Winding Transformers.

The simplified schematic diagram of a three-winding transformer is shown in Figure 8. Labelling the windings in this transformer as high voltage, low voltage and tertiary, the schematic consists of six components, namely:

- the high-to-low voltage winding capacitance ( $C_{H-l}$ ),
- the high-voltage to tertiary winding capacitance ( $C_{H-t}$ ),
- the low-voltage to tertiary winding capacitance ( $C_{L-t}$ ),
- the high-voltage winding to ground capacitance ( $C_{H-g}$ ),
- the low-voltage winding to ground capacitance ( $C_{L-g}$ ), and
- the tertiary-winding to ground capacitance ( $C_{t-g}$ ).

Similarly to the two-winding example, all the capacitances between the windings and ground include the capacitances of the appropriate bushings.

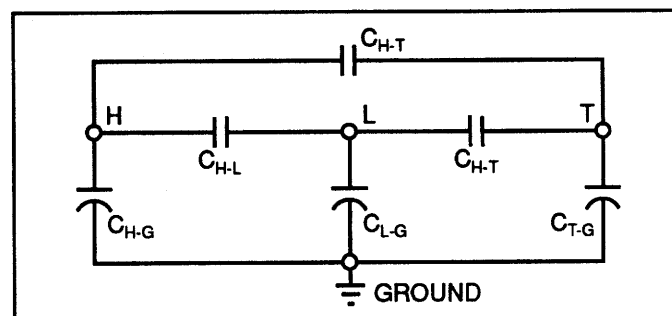


Figure 8. Schematic of a Three-Winding Transformer

### Bushings.

The measurement of bushings is a particular connection of the ungrounded specimen test (UST) connection. The schematic of a typical high-voltage bushing is shown in Figure 9. It consists of:

- high-voltage terminal to Test Tap capacitance ( $C_{H-t}$ ), and
- Test Tap to ground capacitance ( $C_{t-g}$ ).

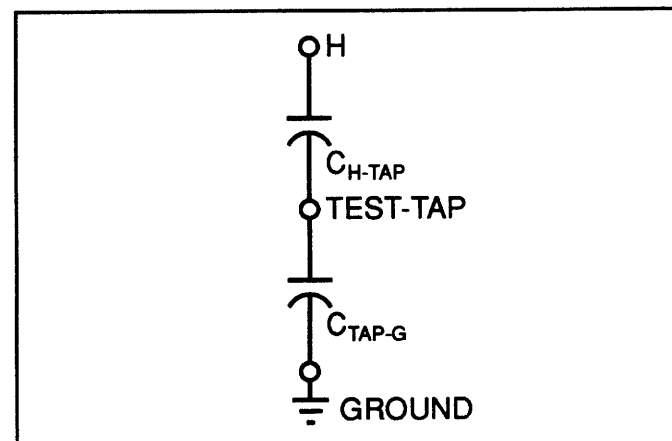


Figure 9. Schematic of a Transformer Bushing

## MAKING THE MEASUREMENTS

Whenever making the measurements, it is important to make ALL the possible measurements. This allows one to double-check all the results on the spot and avoid repeats.

To allow for convenient measurement with the fewest possible set-ups, many commercial test sets provide two measuring leads and a variety of test configurations. With two measuring leads, and calling the instrument connections as High Voltage (HV), Red measuring lead (R), Blue measuring lead (B) and Ground (G), it is possible to make the following measurements:

1. HV - R
2. HV - B
3. HV - (R+B)
4. HV - (G+R+B)
5. HV - G
6. HV - (G+R)
7. HV - (G+B)

The listed measurements offer duplication and allow one to check the results. It is suggested that all of these, plus even additional duplicate readings be taken to ascertain good results.

### Two Winding Transformer.

It is recommended that, typically, fourteen measurements be done on a single-phase two-winding transformer. These measurements would include the following capacitances:

1. H - L (1)
2. H - G (5)
3. H - (L+G) (6)
4. L - H (1)
5. L - G (5)
6. L - (L+G) (6)
7. TapH1 - H1 (1)
8. TapH1 - G (5)
9. TapH2 - H2 (1)
10. TapH2 - G (5)
11. TapL1 - L1 (1)
12. TapL1 - G (5)
13. TapL2 - L2 (1)
14. TapL2 - G (5)

The above sequence assumes that the high-voltage and the low-voltage bushings have test taps. The sequence, although rather long, is not difficult to conduct. The first three measurements are carried out with one connection, the next three with another connection, and the bushing measurements are done two measurements per connection. Therefore six different connections are required to complete the recommended sequence of fourteen measurements.

It is important to point out the intentional duplication of readings that are taken:

- The H-L capacitance is measured twice independently, and another two times together with H-G and L-G.
- The H-G capacitance is measured twice, once alone and once with H-L.
- The L-G capacitance is measured twice, once alone and once with H-L.

The above duplication allows the operator to quickly double-check any reading on the spot. Some of this checking will soon be done by personal computers attached to the test sets.

No double checking of the bushing capacitances are possible. The results of the bushing tests should be very similar and this serves as a check in itself.

As noted above, the capacitance measurements of winding to ground include the capacitance of the associated bushings. If the power factor of the bushings is substantially different from the power factor of the total measurement, then one may wish to

subtract the readings of the bushings from the total in order to obtain the reading of only the winding. One must not forget that there are two bushings per winding on a single-phase transformer, and three or four of them on a three-phase transformer. Again, this calculation is not difficult to do and can be done by the operator on site.

## Three-Winding Transformer

For those who considered the two-winding transformer example to be rather tedious, they will be thrilled by all the readings that are suggested for a three-winding single phase transformer.

Provided that there are bushings to be tested on all three windings of the transformer, then there are 33 tests suggested. These tests measure the following capacitances:

1. H - L (1)
2. H - T (2)
3. H - (L+T) (3)
4. H - (G+L+T) (4)
5. H - G (5)
6. H - (G+L) (6)
7. H - (G+T) (7)
8. L - H (1)
9. L - T (2)
10. L - (H+T) (3)
11. L - (G+H+T) (4)
12. L - G (5)
13. L - (G+H) (6)
14. L - (G+T) (7)
15. T - H (1)
16. T - L (2)
17. T - (H+L) (3)
18. T - (G+H+L) (4)
19. T - G (5)
20. T - (G+H) (6)
21. T - (G+L) (7)
22. TapH1 - H1 (1)
23. TapH1 - G (5)
24. TapH2 - H2 (1)
25. TapH2 - G (5)
26. TapL1 - L1 (1)
27. TapL1 - G (5)
28. TapL2 - L2 (1)
29. TapL2 - G (5)
30. TapT1 - T1 (1)
31. TapT1 - G (5)
32. TapT2 - T2 (1)
33. TapT2 - G (5)

Again, similarly to the two-winding transformer, there are fewer test set-ups as there are readings to be taken. It takes only nine set-ups to do all the 33 tests listed above.

Thus, the first seven readings are taken with the HV lead connected to the H bushing, the next seven with the HV lead connected to the L bushing and the next seven with the HV lead connected to the T bushing. The bushing readings require a different connection for each set of readings for each bushing.

Again one will note the numerous duplications that are suggested. These, together with calculations, will assure that you have a valid set of readings. Each of the main six capacitances are measured twice alone and another six times in combination with other capacitances. This allows for a complete verification of the test results.

Identically to the two-winding transformer situation, if the power factors of the bushings are different from the power factor of the total reading, then the readings of the bushings should be subtracted from the total to obtain the readings of only the winding.

## **Bushings**

The measurement of the bushings is rather simple as there are only two capacitances involved in the measurement. The HV lead is a lead to the test tap which is especially provided on all high-voltage bushings for this reason. The important result here is the Tap-to-conductor capacitance. When in service, it has the system voltage applied to it. The Tap-to-ground capacitance is shorted out during normal operation of the equipment.

One must not forget that if the capacitance of only the winding is required, it is to be calculated by subtracting the capacitance of the bushing from the total capacitance that is measured.

## **SUMMATION**

With the number of readings that need to be taken on the two winding transformer and especially on the three-winding transformer, there is ample opportunity for the test person to make errors in connection, reading or transcription. In order to reduce these to a minimum and to ascertain a good set of test results, first time, every time, some degree of automation is desirable.

The modern automated power factor test sets come to the rescue of the test technician. Such test sets are capable of conducting series of measurements, provide printed records of test results, and when combined with personal computers will double-check every reading that was taken and save it in a database for future reference.